

HY220

Εργαστήριο Ψηφιακών

Κυκλωμάτων

Εαρινό Εξάμηνο
2025


Μηχανές Πεπερασμένων
Καταστάσεων

FSMs




- Οι μηχανές πεπερασμένων καταστάσεων Finite State Machines (FSMs)
 - πιο αφηρημένος τρόπος να εξετάζουμε ακολουθιακά κυκλώματα
 - είσοδοι, έξοδοι, τρέχουσα κατάσταση, επόμενη κατάσταση
 - σε κάθε ακμή του ρολογιού συνδυαστική λογική παράγει τις εξόδους και την επόμενη κατάσταση σαν συναρτήσεις των εισόδων και της τρέχουσας κατάστασης.

Χαρακτηριστικά των FSM

 - Η επόμενη κατάσταση είναι συνάρτηση της τρέχουσας κατάστασης και των εισόδων
- Moore Machine: Οι έξοδοι είναι συνάρτηση της κατάστασης



   - Mealy Machine: Οι έξοδοι είναι συνάρτηση της κατάστασης και των εισόδων




Βήματα Σχεδίασης

- Περιγραφή λειτουργία του κυκλώματος (functional specification)
- Διάγραμμα μετάβασης καταστάσεων (state transition diagram)
- Πίνακας καταστάσεων και μεταβάσεων με συμβολικά ονόματα (symbolic state transition table)
- Κωδικοποίηση καταστάσεων (state encoding)
- Εξαγωγή λογικών συναρτήσεων
- Διάγραμμα κυκλώματος
 - FFs για την κατάσταση
 - ΣΛ για την επόμενη κατάσταση και τις εξόδους

Αναπαράσταση FSM

 
- Καταστάσεις: όλες οι πιθανές τιμές στα ακολουθιακά στοιχεία μνήμης (FFs)
- Μεταβάσεις: αλλαγή κατάστασης
- Αλλαγή τις κατάστασης με το ρολόι αφού ελέγχει την φόρτωση τιμής στα στοιχεία μνήμης (FFs)



- Ακολουθιακή λογική
 - Ακολουθία μέσω μιας σειράς καταστάσεων
 - Βασίζεται στην ακολουθία των τιμών στις εισόδους

Παράδειγμα FSM - Reduce 1s

 
- Αλλαγή του πρώτου 1 σε 0 σε μια σειρά από 1
 - Moore FSM



Moore FSM: General & State

```
module ReduceMoore(
    input logic clk,
    input logic rst,
    input logic in,
    output logic out
);
logic [1:0] current_state; // state register
logic [1:0] next_state;

 // State declarations
parameter int STATE_Zero = 2'h0,
            STATE_One1 = 2'h1,
            STATE_Twos = 2'h2,
            STATE_X = 2'hX;
// Implement the state register
always_ff @(posedge clk) begin
    if (rst) current_state <= STATE_Zero;
    else     current_state <= next_state;
end
```



Moore FSM: Combinatorial


```
always_comb begin
    next_state = current_state; // acts as the default/else
    out = 1'b0;               // default output

    case (current_state)
        STATE_Zero: begin           // last input was a zero
            if (in) next_state = STATE_One1;
        end

        STATE_One1: begin          // we've seen one 1
            if (in) next_state = STATE_Two1s;
            else      next_state = STATE_Zero;
        end

        STATE_Two1s: begin          // we've seen at least 2 ones
            out = 1;
            if (~in) next_state = STATE_Zero;
        end

         default: begin              // in case we reach a bad state
            out = 1'bx;
            next_state = STATE_Zero;
        end
    endcase
end
```




Moore FSM: SystemVerilog Enums

```
module ReduceMooreEnums (
    input logic clk,
    input logic rst,
    input logic in,
    output logic out
);
    enum logic [1:0] {
        STATE_Zero = 2'h0,
        STATE_One1 = 2'h1,
        STATE_Twols = 2'h2 } current_state, next_state;
    // alternative:
    // typedef enum logic [1:0] {
    // STATE_Zero, STATE_One1, STATE_Twols } FSM_State_e;
    // FSM_State_e current_state, next_state;


    // Implement the state register
    always_ff @(posedge clk) begin
        if (rst) current_state <= STATE_Zero;
        else      current_state <= next_state;
    end

```

 


Mealy FSM

```
module ReduceMealy( input logic clk, rst, in, output logic out);  
  
logic current_state; // state register  
logic next_state;  
  
parameter int STATE_Zero = 1'b0,  
        STATE_One1 = 1'b1;  
  
always_ff @(posedge clk) begin  
    if (rst) current_state <= STATE_Zero;  
    else      current_state <= next_state;  
end  
  
always_comb begin  
    next_state = current_state;  
    out = 1'b0;  
    case (current_state)  
        STATE_Zero: if (in) next_state = STATE_One;  
        STATE_One1: begin // we've seen one 1  
            if (~in) next_state = STATE_One;  
            else      next_state = STATE_Zero;  
            Out = In;  
        end  
    endcase  
end  
  
endmodule
```

 

Moore vs Mealy

 


Moore vs Mealy Συμπεριφορά

- Moore
 - απλοποιούν τη σχεδίαση
 - αδυναμία αντίδρασης στις εισόδους στον ίδιο κύκλο - έξοδοι ένα κύκλο μετά
 - διαφορετικές καταστάσεις για κάθε αντίδραση
- Mealy
 - συνήθως λιγότερες καταστάσεις
 - άμεση αντίδραση στις εισόδους – έξοδοι στον ίδιο κύκλο
 - **δυσκολότερη σχεδίαση αφού καθυστερημένη είσοδος παράγει καθυστερημένη έξοδο (μεγάλα μονοπάτια)**
- Η Mealy γίνεται Moore αν βάλουμε καταχωρητές στις εξόδους

Moore Machine σε 1 always block (Bad Idea)

```
module ReduceMoore(
    input logic clk,
    input logic rst,
    input logic in,
    output logic out
);

     logic [1:0] state;          // state register
    parameter int zero = 0,
                one1 = 1,
                two1s = 2;
```




Moore Machine σε 1 always block (Bad Idea)

```
always_ff @ (posedge clk)
  case (state)
    zero: begin
      out <= 0;
      if (in) state <= one1;
      else state <= zero;
    end
    one1:
      if (in) begin
        state <= two1s;
        out <= 1;
      end
      else begin
        state <= zero;
        out <= 0;
      end
    end
    two1s:
      if (in) begin
        state <= two1s;
        out <= 1;
      end
      else begin
        state <= zero;
        out <= 0;
      end
    end
    default: begin
      state <= zero;
      out <= 0;
    end
  endcase
endmodule
```

Οι έξοδοι είναι καταχωρητές


Μπερδεμένο!!!
 Η έξοδος αλλάζει στον
 επόμενο κύκλο

Υλοποίηση FSMs

 

- Προτεινόμενο στυλ υλοποίησης FSM
 - Ο καταχωρητής κατάστασης σε ένα ξεχωριστό always_ff
 - clocked – πάντα reset – χρήση μόνο non-blocking assignment
 - Η συνδυαστική λογική αλλαγής καταστάσεων σε always_comb
 - πάντα default – χρήση μόνο blocking assignments
 - Έξοδοι είτε από always_comb της CL είτε από wires
 - χρήση μόνο blocking assignments (*και σιγουρευτείτε για τις default τιμές*)

Απλή ΦΣΜ

 


Απλή FSM (1/3)

```
module fsm( receive, start, stop,
            error, clk, reset_n);
//  
parameter int C2Q = 1;  
//  
input logic start, stop, error, clk, reset_n;  
output logic receive;  
//  
parameter logic [1:0] IdleState      = 0,  
                  ReceiveState   = 1,  
                  ErrorState    = 2;  
//  
logic [1:0] fsm_state, fsm_nxtstate;  
//  
always_ff @(posedge clk) begin  
    if (~reset_n) fsm_state <= #C2Q IdleState;  
    else          fsm_state <= #C2Q fsm_nxtstate;  
end
```

Απλή FSM (2/3)

```
always_comb begin
    case (fsm_state)
        IdleState:
            begin
                if(error) fsm_nxtstate = ErrorState;
                else begin
                    if(start) fsm_nxtstate = ReceiveState;
                    else fsm_nxtstate = IdleState;
                end
            end
        ReceiveState:
            begin
                if(error) fsm_nxtstate = ErrorState;
                else begin
                    if(stop) fsm_nxtstate = IdleState;
                    else fsm_nxtstate = ReceiveState;
                end
            end
        ErrorState:
            default:
                fsm_nxtstate = IdleState;
    endcase
end
```

 

Απλή FSM (3/3) – Οι έξοδοι

- The Moore Output

```
assign receive = fsm_state[0];
// alternative:
// assign receive = (fsm_state == ReceiveState);
```


- The Mealy Output

```
assign receive = ((fsm_state == IdleState) & start) |
                ((fsm_state == ReceiveState) & ~error & ~stop);

// alternative: with blocking assignments
// always_comb begin
//     receive = 0; // default value for output
//     if ((fsm_state == IdleState) & start)         receive = 1;
//     if ((fsm_state == ReceiveState) & ~error & ~stop) receive = 1;
// end
```

Παράδειγμα: «Αυτόματος Πωλητής» (1/5)

 - Βγάζει αναψυκτικό όταν βάλουμε 15 λεπτά του €
- Κερματοδέκτης για νομίσματα των 5 και 10 λεπτών του €
- Δεν δίνει ρέστα!



Παράδειγμα: «Αυτόματος Πωλητής» (2/5)

- Αναπαράσταση

- Τυπικές είσοδοι:


- 3 των 5¢
 - 5¢, 10¢
 - 10¢, 5¢
 - 2 των 10¢

- Διάγραμμα Καταστάσεων:

- Είσοδοι: in5, in10, reset, clock
 - Έξοδοι: open


- Assumptions:

 - in5 και in10 εμφανίζονται για 1 κύκλο
 - Μένουμε στην ίδια κατάσταση αν δεν έρθει είσοδος
 - Όταν έρθει reset πάμε στην αρχική κατάσταση



Παράδειγμα: «Αυτόματος Πωλητής» (3/5)

 - Ελαχιστοποίηση καταστάσεων - επαναχρησιμοποίηση



present state	inputs		next state	output open
	in10	in5		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	0¢	1
	—	—	—	—

symbolic state table

Παράδειγμα: «Αυτόματος Πωλητής» (4/5)

- Κωδικοποίηση Καταστάσεων – Τυπική

pres. state Q1 Q0	inputs in10 in5		next state D1 D0	output open
0 0	0	0	0 0	0
	0	1	0 1	0
	1	0	1 0	0
	1	1	— —	—
0 1	0	0	0 1	0
	0	1	1 0	0
	1	0	1 1	0
	1	1	— —	—
1 0	0	0	1 0	0
	0	1	1 1	0
	1	0	1 1	0
	1	1	— —	—
1 1	—	—	0 0	1

Παράδειγμα: «Αυτόματος Πωλητής» (5/5)


- Κωδικοποίηση Καταστάσεων – One-hot

present state				inputs		next state				output
Q3	Q2	Q1	Q0	in10	in5	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
						0	0	1	0	0
						0	1	0	0	0
						-	-	-	-	-
0 0 1 0				0	0	0	0	1	0	0
						0	1	0	0	0
						1	0	0	0	0
						-	-	-	-	-
0 1 0 0				0	0	0	1	0	0	0
						0	1	0	0	0
						1	0	0	0	0
						-	-	-	-	-
1	0	0	0	-	-	0	0	0	1	1

Διαγράμματα καταστάσεων – Moore and Mealy


Moore machine

Έξοδοι από κατάσταση

 

Mealy machine

Έξοδοι στις μεταβάσεις

 


Moore Verilog FSM

```
module vending (open, clk, rst, in5, in10);
    input logic clk, rst, in5, in10;
    output logic open;
    logic [1:0] state, next_state;
    parameter int zero = 0, five = 1, ten = 2, fifteen = 3;

    always_comb begin
        open = 0; // default output value
        case (state)
            zero: begin
                if (in5)      next_state = five;
                else if (in10) next_state = ten;
                else          next_state = zero;
                open = 0;
            end
            ...
            fifteen: begin
                next_state = zero;
                open = 1;
            end
            default: begin
                next_state = zero;
                open = 0;
            end
        endcase
    end

     always_ff @ (posedge clk)
        if (rst) state <= zero;
        else      state <= next_state;
endmodule
```



Mealy Verilog FSM

```
module vending (open, clk, rst, in5, in10);
    input logic clk, rst, in5, in10;
    output logic open;
    logic [1:0] state, next_state;
    parameter int zero = 0, five = 1, ten = 2, fifteen = 3;

    always_comb begin
        open = 0; // default output value
        case (state)
            zero: begin
                open = 0;
                if (in10) next_state = ten;
                else if (in5) next_state = five;
                else next_state = zero;
            end
            five: begin
                if (in5) begin
                    next_state = ten;
                    open = 0;
                end
                else if (in10) begin
                    next_state = zero;
                    open = 1;
                end
                else begin
                    next_state = five;
                    open = 0;
                end
            end
            ...
        endcase
    always_ff @ (posedge clk)
        if (!rst) state <= zero;
        else state <= next_state;
    endmodule
```

